 


5. Experiment

5.1 Part A:

Refer to circuit in Figure 1.



a) Refer to the circuit. Derive Boolean expression for output F and G.

$$F = \overline{(\bar{A}(\bar{A}D))}(\bar{A} + BC)$$

$$G = (\bar{A} + BC)(\bar{A}D)$$

b) Simplify equation output F using laws, rules and De Morgan Theorem, and write the equation in Sum of Product (SOP).

$$\begin{aligned} F &= \overline{(\bar{A}(\bar{A}D))}(\bar{A} + BC) \\ &= (\bar{\bar{A}} + \overline{\bar{A}D})(\bar{A} + BC) \\ &= (A + \bar{A}D)(\bar{A} + BC) \\ &= A\bar{A} + ABC + \bar{A}\bar{A}D + \bar{A}BCD \\ &= ABC + \bar{A}\bar{A}D + \bar{A}BCD \\ &= ABC + \bar{A}D + \bar{A}BCD \end{aligned}$$

c) Simplify equation output G using laws, rules and De Morgan Theorem, and write the equation in Product of Sum (POS).

$$G = (\bar{A} + BC)(\overline{AD})$$

$$= (\bar{A} + BC)(\bar{A} + \bar{D})$$

$$= (\bar{A} + BC)(A + \bar{D})$$


$$= (\bar{A} + B)(\bar{A} + C)(A + \bar{D})$$


Simulate the circuit and construct the truth table and complete the following.

Truth table for output circuit F and G shown in Figure 1

Input				Output	
A	B	C	D	F	G
0	0	0	0	0	1
0	0	0	1	1	0
0	0	1	0	0	1
0	1	0	1	1	0
0	1	0	0	0	1
0	1	1	1	1	0
0	1	1	0	0	1
1	0	0	1	1	0
1	0	0	0	0	0
1	0	1	1	0	0
1	0	1	0	0	0
1	1	0	1	0	0
1	1	0	0	0	0
1	1	1	1	0	0
1	1	1	0	1	1
1	1	1	1	1	1

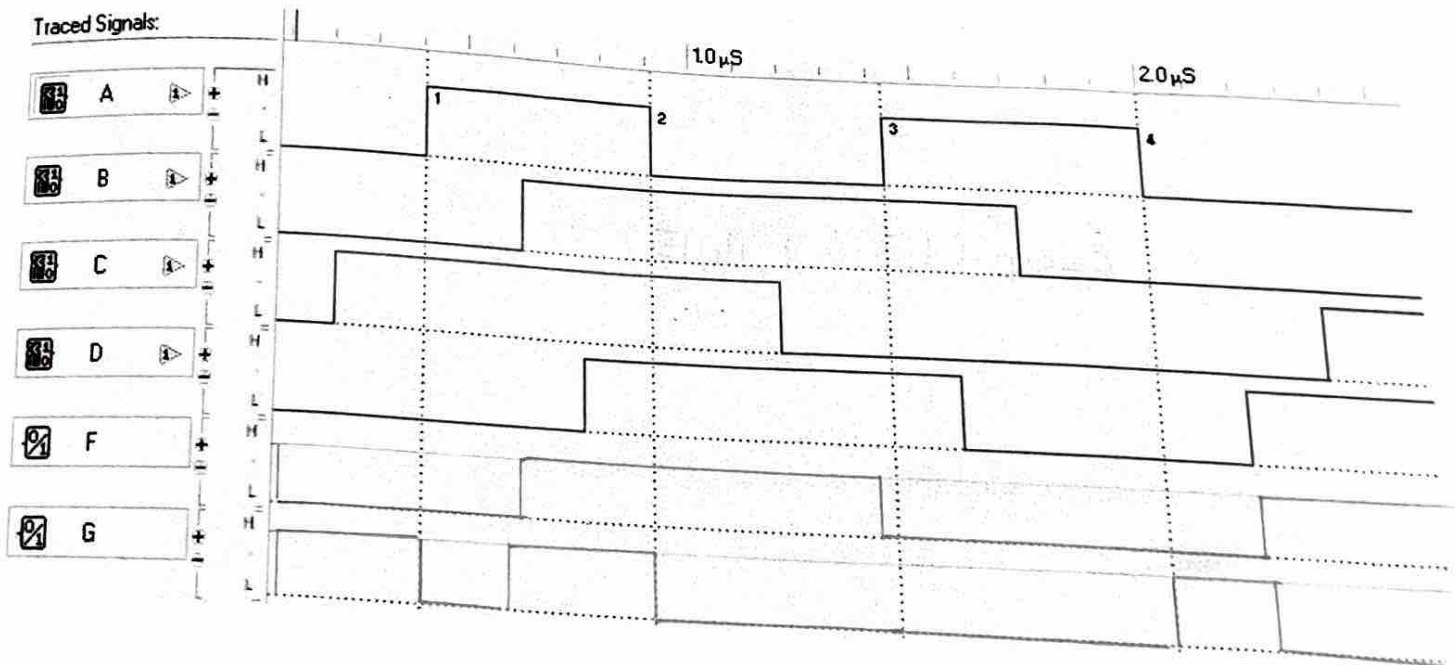d) Using Deeds, draw circuit in Figure 1. Simulate and complete the waveform output F and G by referring the following diagram:



 

e) Write Boolean equation for output F using Sigma notation.

$$\Sigma_{ABCD} (1, 3, 5, 7, 14, 15)$$

f) Write Boolean equation for output G using Pi notation.

$$\Pi_{ABCD} (1, 3, 5, 7, 8, 9, 10, 11, 12, 13)$$

Experimental steps

- i) Construct Truth Table in Table 1 for the LRT operations. Use variables S , $S1$, $S2$, and $S3$ as INPUTS and $OPEN$ and $ALARM$ as OUTPUTS.

Table 1

INPUT				OUTPUT	
S	S1	S2	S3	OPEN	ALARM
0	0	0	0	0	0
0	0	0	1	0	1
0	0	1	0	0	1
0	0	1	1	0	0
0	1	0	0	0	1
0	1	0	1	0	0
0	1	1	0	0	0
0	1	1	1	0	0
1	0	0	0	0	1
1	0	0	1	1	0
1	0	1	0	1	0
1	0	1	1	0	0
1	1	0	0	1	0
1	1	0	1	0	0
1	1	1	0	0	0
1	1	1	1	0	0

- ii) Use K-Map to get optimized SOP Boolean equations for the $OPEN$ and $ALARM$ circuits

$OPEN$

$AB \backslash CD$	00	01	11	10
00	0	0	0	0
01	0	0	0	0
11	1	0	0	0
10	0	1	0	1

$$= AB\bar{C}\bar{D} + A\bar{B}\bar{C}D + A\bar{B}C\bar{D}$$

Experimental steps

- i) Construct Truth Table in Table 1 for the LRT operations. Use variables S , $S1$, $S2$, and $S3$ as INPUTS and $OPEN$ and $ALARM$ as OUTPUTS.

Table 1

INPUT				OUTPUT	
S	S1	S2	S3	OPEN	ALARM
0	0	0	0	0	0
0	0	0	1	0	1
0	0	1	0	0	1
0	0	1	1	0	0
0	1	0	0	0	1
0	1	0	1	0	0
0	1	1	0	0	0
0	1	1	1	0	0
1	0	0	0	0	1
1	0	0	1	1	0
1	0	1	0	1	0
1	0	1	1	0	0
1	1	0	0	1	0
1	1	0	1	0	0
1	1	1	0	0	0
1	1	1	1	0	0

- ii) Use K-Map to get optimized SOP Boolean equations for the $OPEN$ and $ALARM$ circuit

$OPEN$

$AB \backslash CD$	00	01	11	10
00	0	0	0	0
01	0	0	0	0
11	1	0	0	0
10	0	1	0	1



$$= AB\bar{C}\bar{D} + A\bar{B}\bar{C}D + A\bar{B}C\bar{D}$$

ALARM

CD \ AB	00	01	11	10
00	0	1	0	1
01	1	0	0	0
11	0	0	0	0
10	1	0	0	0

$$= \bar{A}\bar{B}\bar{C}\bar{D} + \bar{A}\bar{B}\bar{C}D + A\bar{B}\bar{C}\bar{D} + \bar{A}\bar{B}C\bar{D}$$

  iii) From equations in (ii), draw your final *OPEN* and *ALARM* circuits using Deeds Simulator.



- iv) Simulate the circuit design in (iii) and construct Truth Table in Table 2.

Table 2


INPUT				OUTPUT	
S	S1	S2	S3	OPEN	ALARM
0	0	0	0	0	0
0	0	0	1	0	1
0	0	1	0	0	1
0	0	1	1	0	0
0	1	0	0	0	1
0	1	0	1	0	0
0	1	1	0	0	0
0	1	1	1	0	0
1	0	0	0	0	1
1	0	0	1	1	0
1	0	1	0	1	0
1	0	1	1	0	0
1	1	0	0	1	0
1	1	0	1	0	0
1	1	1	0	0	0
1	1	1	1	0	0

Compare the answer of Table 2 and Table 1. What is your conclusion?


Both output on Table 2 and Table 1 are equivalent.

- v) Use dual symbol to convert, AND-OR circuit to NAND gates only. Draw the final circuit using Deeds Simulator.

OPEN

 

ALARM

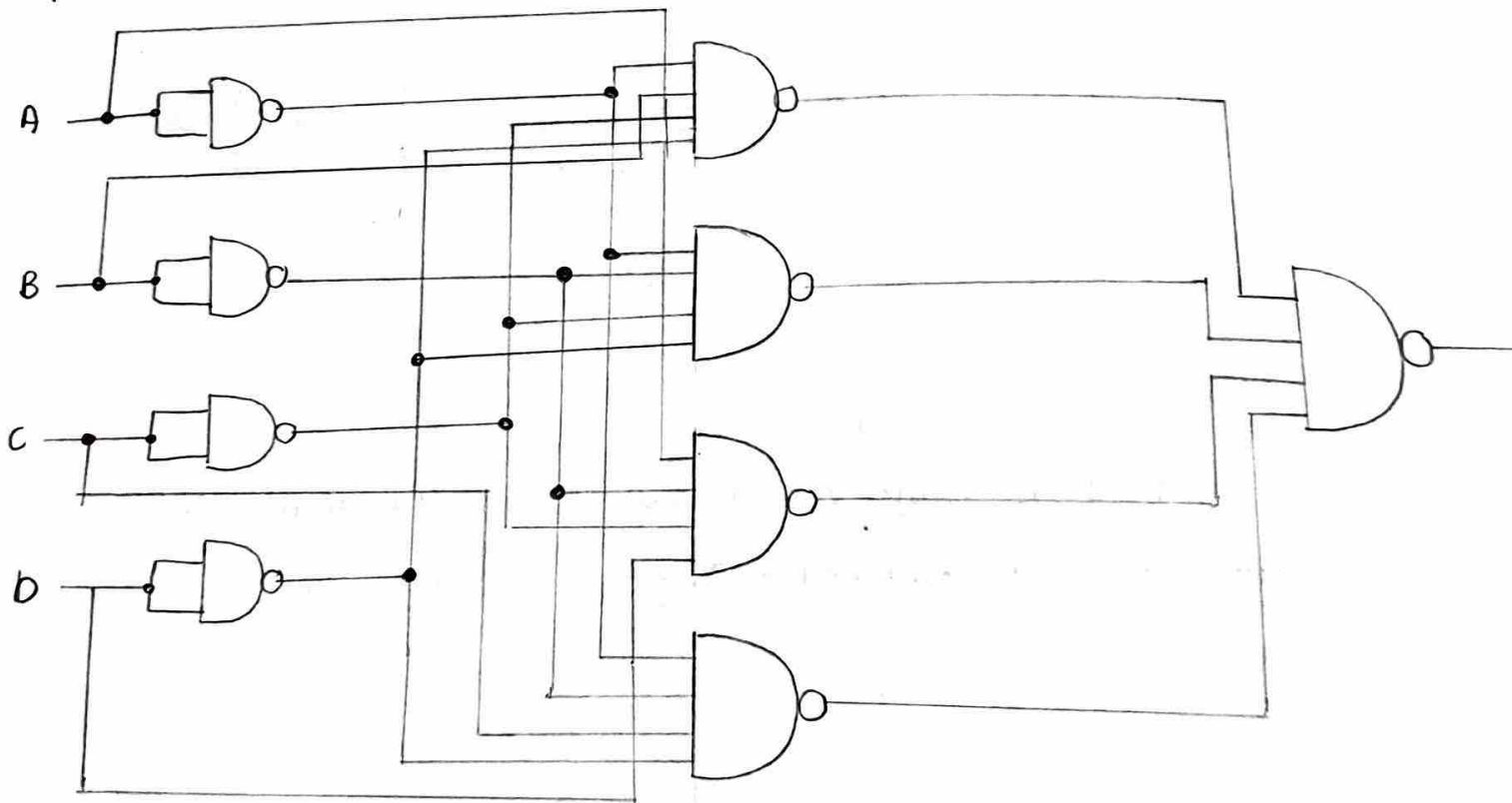

vi) Simulate the final NAND gates design in (v) and construct Truth Table in Table 3.

Table 3

INPUT				OUTPUT	
S	S1	S2	S3	OPEN	ALARM
0	0	0	0	0	0
0	0	0	1	0	1
0	0	1	0	0	1
0	0	1	1	0	0
0	1	0	0	0	1
0	1	0	1	0	0
0	1	1	0	0	0
0	1	1	1	0	0
1	0	0	0	0	1
1	0	0	1	1	0
1	0	1	0	1	0
1	0	1	1	0	0
1	1	0	0	1	0
1	1	0	1	0	0
1	1	1	0	0	0
1	1	1	1	0	0

Compare the answer of Table 2 and Table 3. What is your conclusion?

The output in Table 2 and Table 3 are equivalence. Thus,
NAND gate and ~~and~~ AND-OR gate are equivalence.



Fully Completed ☐

Partially Completed ☐

Checked by: _____